 


LAB 1: BCD-7segment Decoder

Date: 7 de mayo de 2025



Proffesor: Dr. Francisco Javier Rodríguez Navarrete

Students: Cesar Eduardo Inda Cenicerros

Alonso Emmanuel López Macías

Team: 14

Introduction

This lab focuses on the design and implementation of a BCD to 7-segment display decoder using an FPGA as the development platform. Decoders are fundamental digital circuits that identify specific combinations of input bits and generate corresponding outputs based on defined conditions. In this case, the system receives a binary-coded decimal (BCD) input and converts it into a human-readable representation using 7-segment displays, which are commonly used in embedded systems. The objective of this activity is to help students understand the usefulness of decoders in digital hardware, strengthen their logic design skills, and become familiar with the Double Dabble encoding technique used to represent numbers greater than a single decimal digit. The programming was carried out using the language studied during the course, Verilog HDL, with the aim of continuing to practice its syntax and hardware-oriented structure. This allowed for the implementation of each required design throughout the course, applying different programming approaches and adhering to best practices in hardware description using this language.

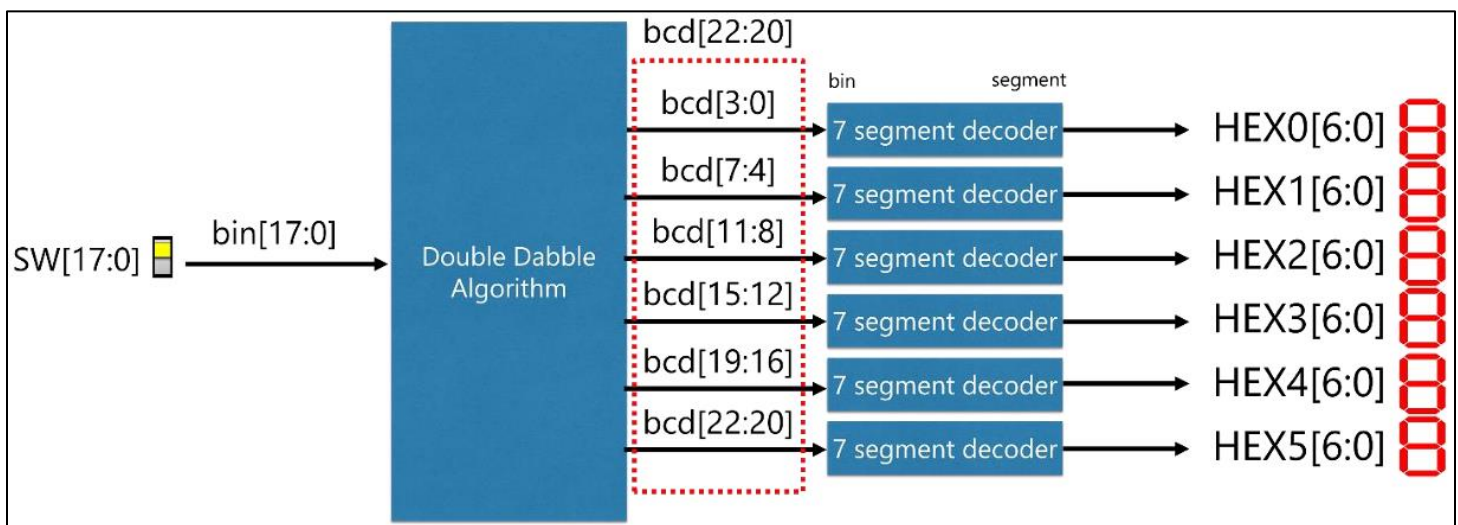


Figure: 1 Decoder - Bcd 7 Segment

Requirements

Step1.- The DE2-115 7 segment displays are common anode, this means that the corresponding connected line must be set to 0 in order for the display to light up that segment.

Step2.- Connect the 4-bit input to the 4-bit output of the double dabble algorithm that can split any number from 0 to 9,999,999, and use the 18 slide switches to represent any number from 0 to 262,143 as the input of the double dabble algorithm.

Step3.- The circuit should look a bit.

Step4.- Implement the circuit on the FPGA.

- Use the following switches for input bin: SW [17] to SW [0]
- Use the following 7 segment displays for outputs: HEX7 to HEX0

Development

The first step was to create the main logic of the practice, is the main entity.

```
/*Este corresponde al modulo principal de la practica, debe estar en top entity
Aqui se conectan los switches a la entrada de los displays de 7 segmentos*/

module top(
    input [17:0] SW, //Entradas de los 18 switches si esta todo alto es: "262143"
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6 //Salida 7 displays de 7 segmentos (hex0 a hex6)
);
    wire [3:0] bcd [6:0]; //Este es un arreglo de 7 digitos del bcd a los 4 bits bcd0 a bcd6

    //Esta es una instancia de modulo que convierte el binario a bcd
    binary_to_bcd converter(
        .binary(SW), //entrada binaria 18 bits a los switches
        .bcd6(bcd[6]), //digito más significativo (centenas de millar)
        .bcd5(bcd[5]),
        .bcd4(bcd[4]),
        .bcd3(bcd[3]),
        .bcd2(bcd[2]),
        .bcd1(bcd[1]),
        .bcd0(bcd[0]) //digito menos signitico (unidades)
    );

    //Instancia de decodificador bcd 7segmentos para cada digito
    bcd_to_7seg disp0(.bcd(bcd[0]), .seg(HEX0)); //unidades
    bcd_to_7seg disp1(.bcd(bcd[1]), .seg(HEX1)); //decenas
    bcd_to_7seg disp2(.bcd(bcd[2]), .seg(HEX2)); //centenas
    bcd_to_7seg disp3(.bcd(bcd[3]), .seg(HEX3)); //unidades de mil
    bcd_to_7seg disp4(.bcd(bcd[4]), .seg(HEX4)); //decenas de mil
    bcd_to_7seg disp5(.bcd(bcd[5]), .seg(HEX5)); //centenas de mil
    bcd_to_7seg disp6(.bcd(bcd[6]), .seg(HEX6)); //millón (solo mostrara 0,1,2 en este caso)
endmodule
```

Figure: 2 Module Top

The next aspect to consider is the part of the module that converts the 18-bit binary value into the 7 BCD digits using the Double Dabble algorithm, in order to generate the required binary inputs and logical shifts.

```
//Este modulo convierte el binario de 18 bits a 7 digitos bcd usando el "double dabble"
module binary_to_bcd(
  input [17:0] binary, //entrada binaria de 18 bits (valor maximo = 262143)
  output reg [3:0] bcd6, bcd5, bcd4, bcd3, bcd2, bcd1, bcd0 //salidas 7 digitos bcd a 4 bits de cada uno
);
  integer i;
  reg [55:0] shift_reg; //registro de desplazamiento 18 bits de entrada + 7*4 bits BCD = 46, se usan 56 bits por seguridad

  always @(*) begin
    shift_reg = 56'b0; //se inicializa el registro a 0
    shift_reg[17:0] = binary; //se coloca el numero binario en los bits menos significativos

    //aqui el double dabble se ejecutara 18 ciclos
    for (i = 0; i < 18; i = i + 1) begin

      //aqui se corrige el bcd si es >=5 antes de desplazar
      if (shift_reg[21:18] >= 4'd5) shift_reg[21:18] = shift_reg[21:18] + 4'd3;
      if (shift_reg[25:22] >= 4'd5) shift_reg[25:22] = shift_reg[25:22] + 4'd3;
      if (shift_reg[29:26] >= 4'd5) shift_reg[29:26] = shift_reg[29:26] + 4'd3;
      if (shift_reg[33:30] >= 4'd5) shift_reg[33:30] = shift_reg[33:30] + 4'd3;
      if (shift_reg[37:34] >= 4'd5) shift_reg[37:34] = shift_reg[37:34] + 4'd3;
      if (shift_reg[41:38] >= 4'd5) shift_reg[41:38] = shift_reg[41:38] + 4'd3;
      if (shift_reg[45:42] >= 4'd5) shift_reg[45:42] = shift_reg[45:42] + 4'd3;

      shift_reg = shift_reg << 1; //se hace un desplazamiento a la izquierda (con el bit nuevo)
    end
    //se extraen los 7 digitos del bcd del registro
    bcd6 = shift_reg[45:42]; //digito mas significativo
    bcd5 = shift_reg[41:38];
    bcd4 = shift_reg[37:34];
    bcd3 = shift_reg[33:30];
    bcd2 = shift_reg[29:26];
    bcd1 = shift_reg[25:22];
    bcd0 = shift_reg[21:18]; //digito menos significativo
  end
endmodule
```

Figure: 3 Module Binary-Bcd

After that, the module responsible for converting a 4-bit BCD value to a 7-segment output for a common anode display was defined. This section includes part of the always block mechanism used to handle the different display segment cases.

```
/*Este modulo convierte un digito bcd de 4bits a un valor de 7 seg
es decir enciende con "0"*/
module bcd_to_7seg(
  input [3:0] bcd,
  output reg [6:0] seg // "a" la "g" (segmentos del display)
);
  always @(*) begin
    case (bcd)
      4'd0: seg = 7'b1000000; // 0
      4'd1: seg = 7'b1111001; // 1
      4'd2: seg = 7'b0100100; // 2
      4'd3: seg = 7'b0110000; // 3
      4'd4: seg = 7'b0011001; // 4
      4'd5: seg = 7'b0010010; // 5
      4'd6: seg = 7'b0000010; // 6
      4'd7: seg = 7'b1111000; // 7
      4'd8: seg = 7'b0000000; // 8
      4'd9: seg = 7'b0010000; // 9
      default: seg = 7'b1111111; //se apaga el display si el
    endcase
  end
endmodule
```

Figure: 4 Module bcd-7segment

Testbench

On this occasion, the code was loaded directly onto the FPGA board; therefore, a testbench was not used.

FPGA Implementation

Once the program was completed, the compilation process was carried out in order to generate the pin assignment plan and correctly map the pins according to the program's requirements.

Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat May 10 20:00:35 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	top
Top-level Entity Name	top
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	220 / 114,480 (< 1 %)
Total registers	0
Total pins	67 / 529 (13 %)
Total virtual pins	0
Total memory bits	0 / 3,981,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 532 (0 %)
Total PLLs	0 / 4 (0 %)

Figure: 5 Compilation Brief

Then the pines were assigned

Node Name	Direction	Location	Node Name	Direction	Node Name	Direction
out HEX0[6]	Output	PIN_H22	out HEX3[6]	Output	out HEX5[6]	Output
out HEX0[5]	Output	PIN_J22	out HEX3[5]	Output	out HEX5[5]	Output
out HEX0[4]	Output	PIN_L25	out HEX3[4]	Output	out HEX5[4]	Output
out HEX0[3]	Output	PIN_L26	out HEX3[3]	Output	out HEX5[3]	Output
out HEX0[2]	Output	PIN_E17	out HEX3[2]	Output	out HEX5[2]	Output
out HEX0[1]	Output	PIN_F22	out HEX3[1]	Output	out HEX5[1]	Output
out HEX0[0]	Output	PIN_G18	out HEX3[0]	Output	out HEX5[0]	Output
out HEX1[6]	Output	PIN_U24	out HEX4[6]	Output	out HEX6[6]	Output
out HEX1[5]	Output	PIN_U23	out HEX4[5]	Output	out HEX6[5]	Output
out HEX1[4]	Output	PIN_W25	out HEX4[4]	Output	out HEX6[4]	Output
out HEX1[3]	Output	PIN_W22	out HEX4[3]	Output	out HEX6[3]	Output
out HEX1[2]	Output	PIN_W21	out HEX4[2]	Output	out HEX6[2]	Output
out HEX1[1]	Output	PIN_Y22	out HEX4[1]	Output	out HEX6[1]	Output
out HEX1[0]	Output	PIN_M24	out HEX4[0]	Output	out HEX6[0]	Output
out HEX2[6]	Output	PIN_W28				
out HEX2[5]	Output	PIN_W27				
out HEX2[4]	Output	PIN_Y26				
out HEX2[3]	Output	PIN_W26				
out HEX2[2]	Output	PIN_Y25				
out HEX2[1]	Output	PIN_AA26				
out HEX2[0]	Output	PIN_AA25				

in SW[17]	Input	PIN_Y23
in SW[16]	Input	PIN_Y24
in SW[15]	Input	PIN_AA22
in SW[14]	Input	PIN_AA23
in SW[13]	Input	PIN_AA24
in SW[12]	Input	PIN_AB23
in SW[11]	Input	PIN_AB24
in SW[10]	Input	PIN_AC24
in SW[9]	Input	PIN_AB25
in SW[8]	Input	PIN_AC25
in SW[7]	Input	PIN_AB26
in SW[6]	Input	PIN_AD26
in SW[5]	Input	PIN_AC26
in SW[4]	Input	PIN_AB27
in SW[3]	Input	PIN_AD27
in SW[2]	Input	PIN_AC27
in SW[1]	Input	PIN_AC28
in SW[0]	Input	PIN_AB28

Figure: 6 Pin Planner

The RTL view can be observed as follows.

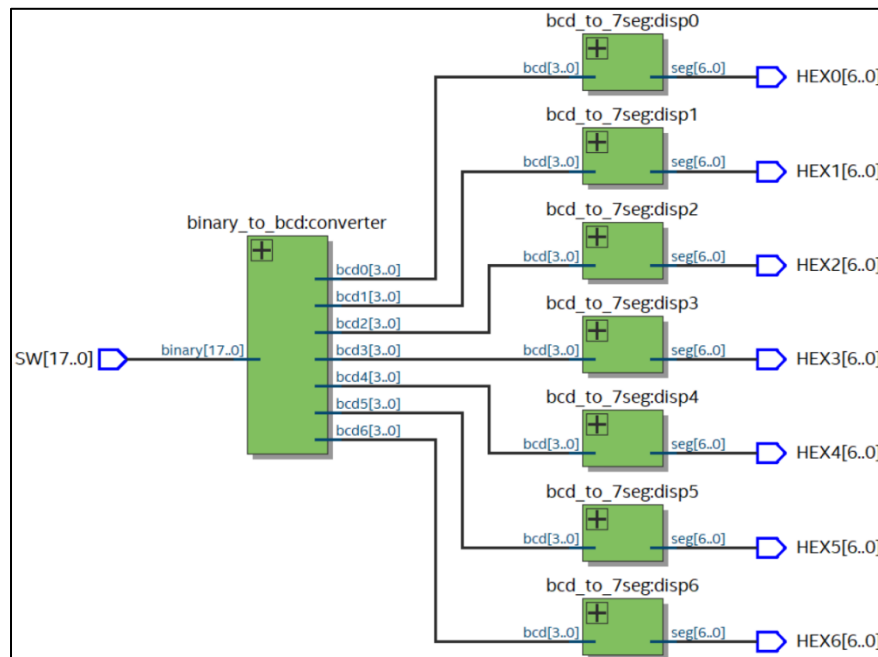


Figure: 7 RTL

GitHub Repository

https://github.com/CeicGitHub/Fundamentals_Of_Digital_Design_FPGA_2/tree/Lab1_BcdDecoder

Conclusion / Issues

Cesar Eduardo Inda Cenicerros

Some of the challenges I faced while completing this lab involved understanding how to properly create the instances within the BCD decoder. Unlike previous labs from the first module, where we only had to consider values from 0 to 15, this time we needed to handle a much wider range—from units up to the millions. Another complex part was understanding the Double Dabble algorithm and correctly implementing the for loop to execute the required number of shifts. It was also challenging to manage the shifting operations and to grasp the purpose and usage of the 56-bit register defined as “reg [55:0]”. Personally, I had previous experience programming in Verilog thanks to a former master's colleague from ITESO who worked at Intel. However, I had not had the opportunity to explore the deeper conceptual aspects, including the use of testbenches covered in other labs. Through this project, I learned more about logic design and realized that there are multiple ways to achieve the same functionality on an FPGA. I also gained a clearer understanding of the Double Dabble algorithm and how to leverage multiple modules throughout a project to support implementation.

Alonso Emmanuel Lopez Macias

This practice personally allowed me to deepen my understanding of Verilog. It became much clearer to me that programming is not limited to the method we used previously with BDF diagrams in the earlier module. I also realized how certain instructions can be defined within the code—for example, the use of integer in this lab for the for loop, which is similar to how it is used in C. Additionally, the concept of shifting operations became clearer to me, as did the use of the always block to create sequential or conditional behavior. In the context of registers and event-driven logic, this block plays a crucial role. I also understood that, because this was a more complex and robust implementation, the learning impact was greater compared to previous labs.